

FPGA PROJECT – QUADRATIC SOLVER

Quinlan Missikowski

Description

This project using the DE10 Lite board will showcase the functionality of a quadratic equation solver. The board will compute the approximate real roots of the function given by the user.

Uses of Combinational and Sequential Logics

- Combinational logic must be used to implement the various functions needed to calculate the real roots, such as:
 - Adder/subtractor circuits.
 - Multiplier/divisor circuits.
- Sequential logic is used to optimize the user input experience when inserting the quadratic equation. A FSM is used to increment the state of the circuit representing each stage of the user input and the displaying of the calculated result.

Testable Features

- User interface used to create the values needed for the quadratic equation:

$$y = Ax^2 + Bx + C$$

- For parameters A, B and C, the user can set these values by toggling the switches representing each 7.S.D, and then increment/decrement the selected 7.S.Ds using buttons.
- Display calculations from the user inputs using the quadratic formula:
$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$
 - On the 7.S.Ds, display the correct value for $B^2 - 4AC$ and $\sqrt{B^2 - 4AC}$.
 - On the 7.S.Ds, display the real root(s) of the inserted quadratic function: X_1 & X_2 , or display “NRR” if there are no real roots.

Results

Video Demo: https://youtu.be/hSoHo_MV8Y4